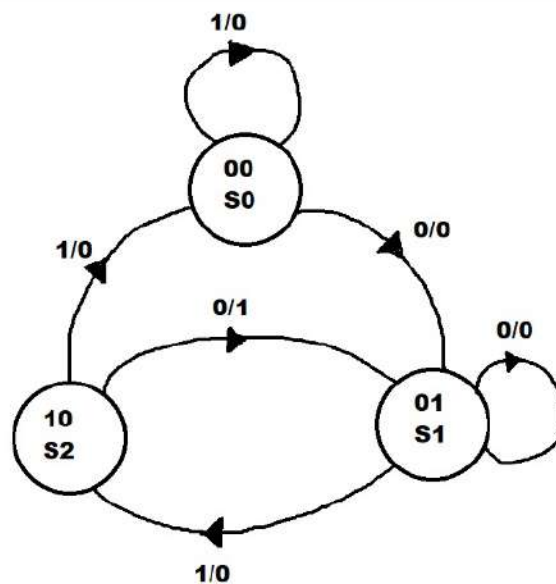


INPUT:

x- Continuous string of binary digits.

OUTPUT:

y- It becomes 1 when sequence 010 gets detected.

**STATES:**

S0: Idle State, remains in this state when first digit of sequence, i.e. 0 is not detected (010)

S1: This state is achieved as soon as first digit is detected, i.e. 0 in 010.

S2: This state is achieved as soon as second digit i.e. 1 is detected (010)

Present State		Input	Next State		Flip Flop Input		Output
Qa	Qb	x	Qa+	Qb+	Ta	Tb	y
0	0	1	0	0	0	0	0
0	0	0	0	1	0	1	0
0	1	0	0	1	0	0	0
0	1	1	1	0	1	1	0
1	0	0	0	1	1	1	1
1	0	1	0	0	1	0	0

